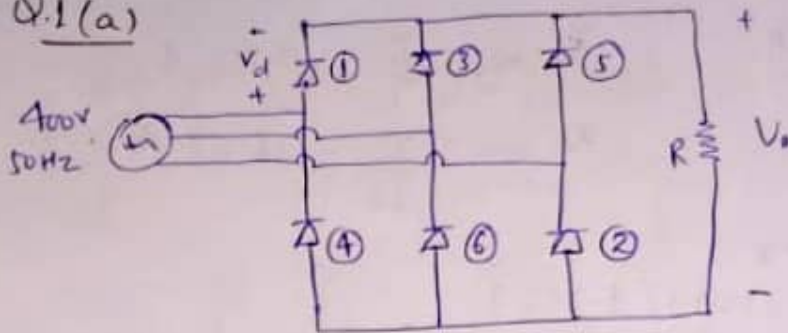


Assignment - 3

Roll no - 24M1355
ADITYA KUMAR

Q.1(a)




$$P_{out} = 15 + w$$

$$\begin{aligned} \text{Avg } V_o &= \frac{3 V_{m\phi}}{\pi} \\ &= \frac{3 \times 400 \sqrt{2}}{\pi} = 540.189 \text{ V} \end{aligned}$$

$$\text{Avg } I_o = \frac{15000}{540.189} = 27.768 \text{ A}$$
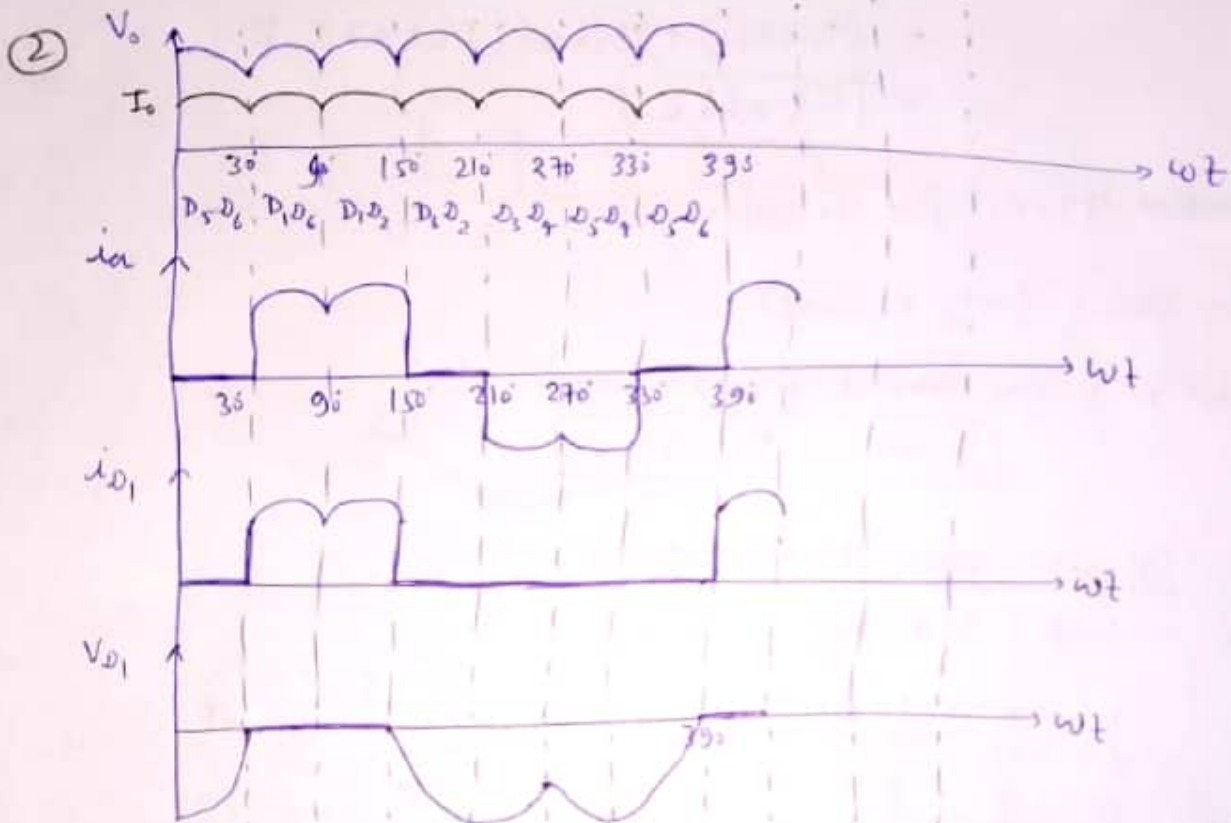
$$R = \frac{(540.189)^2}{15000} = 19.4536 \Omega$$



$30^\circ < \omega t < 90^\circ$	Diode ON $V_{D1} = 0$
$90^\circ < \omega t < 150^\circ$	Diode ON : $V_{D1} = 0$
$150^\circ < \omega t < 210^\circ$	$V_{D1} = V_b - V_a = -V_{ab}$
$210^\circ < \omega t < 270^\circ$	$V_{D1} = V_b - V_a = -V_{ab}$
$270^\circ < \omega t < 330^\circ$	$V_{D1} = V_c - V_a = +V_{ca}$
$330^\circ < \omega t < 390^\circ$	$V_{D1} = V_c - V_a = +V_{ca}$

③ Power loss in complete diode bridge module = ?

$$\begin{cases} V_{th} = 1.04 \\ R_{D, on} = 6 \text{ m}\Omega \end{cases} \text{ at } I = 20 \text{ A}$$

$$I_{D, avg} = \frac{I_o}{3} = 9.256 \text{ A}$$

$$I_{D, rms} = \frac{I_o}{\sqrt{3}} = 16.03 \text{ A}$$

$$\begin{aligned} P_{cond} &= I_{D, rms}^2 R_{D, on} + V_{th} I_{D, avg} \\ &= (16.03)^2 \cdot (0.006) + (1.04)(9.256) \\ &= 11.168 \text{ W} \end{aligned}$$

$$P_{sw} = 0 \quad \therefore P_{total} = 11.168 \text{ W} \quad (\text{for 1 diode})$$

$$P_{total \text{ bridge}} = 11.168 \times 6 = \boxed{67.010 \text{ W}} \quad \underline{\text{Ans}}$$

$$\begin{aligned} \text{Junction temp } T_j &= T_a + P \cdot R_{thermal} \quad \dots \{ T_a = 40^\circ\text{C} \} \\ &= (40 + 273) + (11.168)(1.1 + 0.07) \text{ K} \\ &= \boxed{53.066^\circ\text{C}} \end{aligned}$$

④ ~~Partial~~ PLECS file is uploaded.


⑤ In case-1 (only R load)

Total RMS line current from AC source

$$\boxed{I_{s, rms} = 22.693 \text{ A}} \quad \underline{\text{Ans}}$$

Case-b Capacitor across the DC link :-

Given: Peak to peak ripple = 10 V

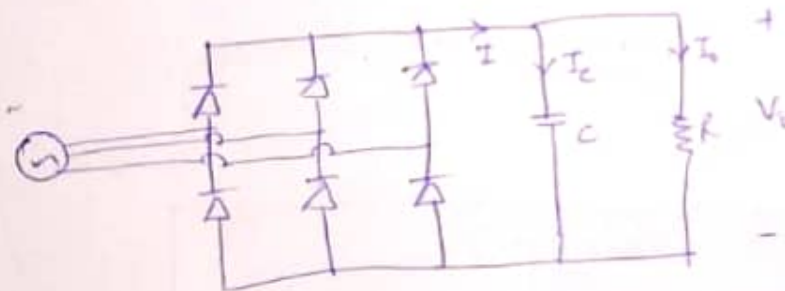


$$I_c = C \frac{dv_c}{dt}$$

$$C = \frac{I_c}{\Delta v \cdot 6f}$$

$$= \frac{27.76}{10 \times 6 \times 50}$$

$$\boxed{C = 9.253 \text{ mF}}$$

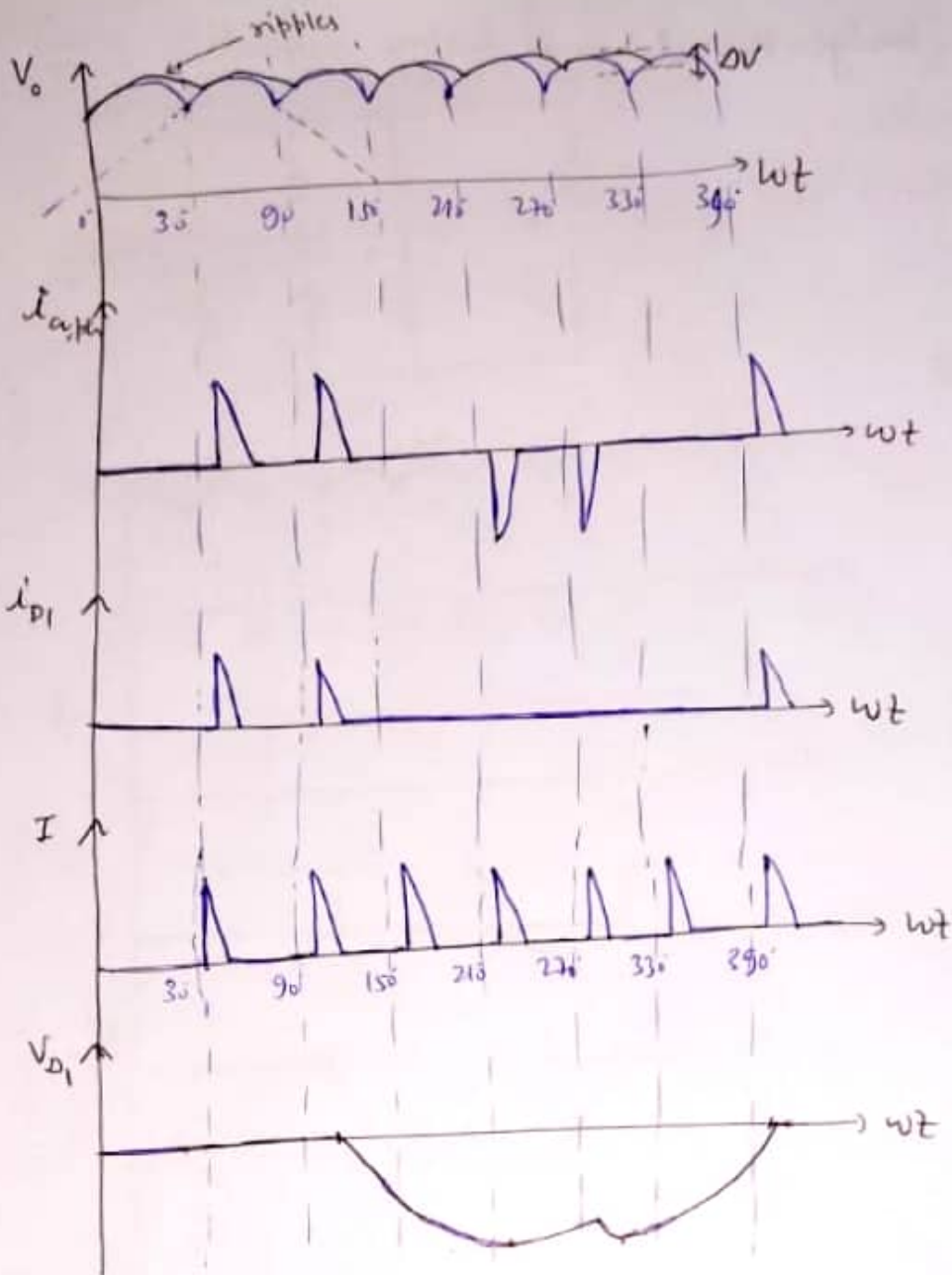

$$30^\circ < \omega t < 90^\circ \quad V_{D1} = 0$$

$$210^\circ < \omega t < 330^\circ \quad V_{D1} = -V_{ac}$$

$$V_{D1} + V_{D4} = -V_o \quad \text{--- (1)}$$

$$V_{D3} + V_{D5} = -V_o \quad \text{--- (2)}$$


$$V_{D5} + V_{D6} = -V_o \quad \text{--- (3)}$$

$$V_{D1} - V_{D3} = V_{ac} \quad \text{--- (4)}$$

$$V_{D3} - V_{D5} = V_{ac} \quad \text{--- (5)}$$


$$V_{D1} - V_{D5} = V_{ac} \quad \text{--- (6)}$$

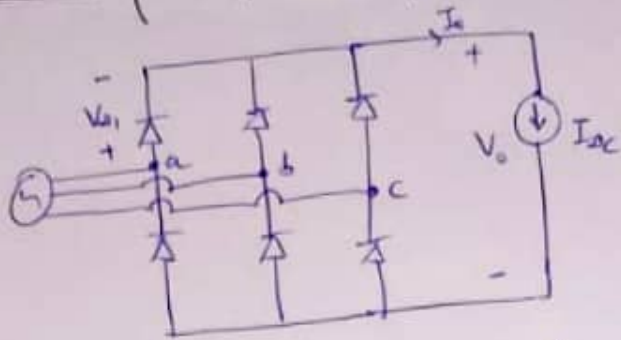Case-c (Rectifier output current = Constant)



$$V_s = 540.189 \text{ V}$$

$$I_o = 27.76 \text{ A (fixed)}$$

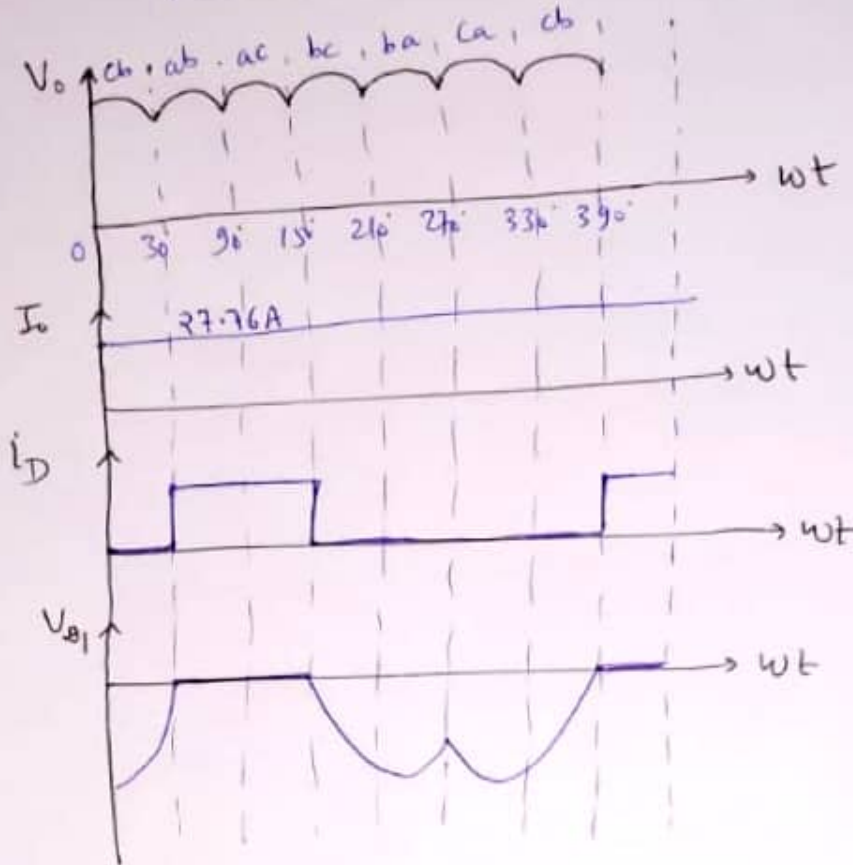

$$I_{o1} = I_o \text{ for } 30^\circ < \omega t < 150^\circ$$

$$I_{o1, \text{avg}} = \frac{I_o}{3} = 9.256 \text{ A}$$

$$I_{o1, \text{rms}} = \frac{I_o}{\sqrt{3}} = 16.03 \text{ A}$$

$$\begin{cases} V_{th} = 1.04 & \text{at } I = 20 \text{ mA} \\ R_{o, \text{on}} = 6 \text{ m}\Omega \\ \text{from datasheet} \end{cases}$$

$$P_{\text{cond}} = V_{th} \cdot I_{o1, \text{avg}} + I_{o1, \text{rms}}^2 \cdot R_{th}$$

$$= 1.04 \times 9.256$$

$$+ (16.03)^2 \times 0.006$$

$$= 11.168 \text{ W}$$

$$P_{\text{sw}} \approx 0$$

$$P_{\text{total bridge}} = 6 \times 11.168 = \boxed{67.01 \text{ W}}$$

$$T_j = T_a + R_{\text{thermal}} \cdot P = \boxed{53.066^\circ \text{C}}$$

$30^\circ < \omega t < 90^\circ$	Diode ON : $V_{o1} = 0$
$90^\circ < \omega t < 150^\circ$	Diode ON : $V_{o1} = 0$
$150^\circ < \omega t < 210^\circ$	$V_{o1} = V_b - V_a = -V_{ab}$
$210^\circ < \omega t < 270^\circ$	$V_{o1} = V_b - V_a = -V_{ab}$
$270^\circ < \omega t < 330^\circ$	$V_{o1} = V_c - V_a = +V_{ca}$
$330^\circ < \omega t < 390^\circ$	$V_{o1} = V_c - V_a = +V_{ca}$

$$\cdot \text{RMS line current from source} = \boxed{22.67 \text{ A}}$$

Ans